

HD44780 CHARACTER LCD DISPLAYS – PART 1

🕒 March 9, 2010 📁 [Input/Output Devices, Tutorials](#) 💬 14 Comments

Introduction


LCD character displays can be found in espresso machines, laser printers, children's toys and maybe even the odd toaster. The Hitachi HD44780 controller has become an industry standard for these types of displays. This tutorial will teach you the basics of interfacing with a HD44780 compatible display using some DIP switches and a few other components.

Pinout

The module that we are using is a 16 character x 2 line display that we stock [over here](#). It uses an ST7065C controller, which is HD44780 compatible. The figure below shows the LCD module and pinout.

✕


[Privacy Preferences](#)[I Agree](#)

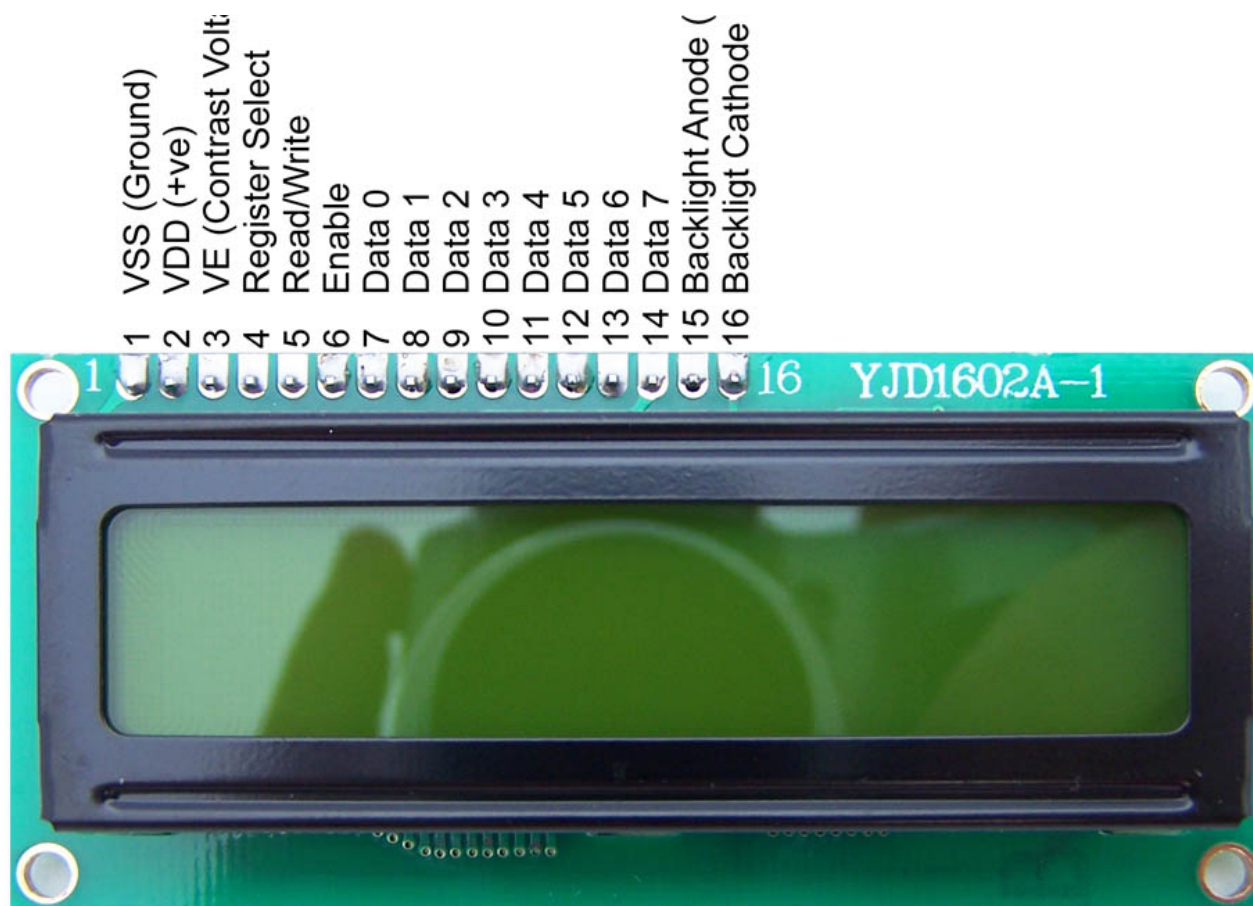

The last 2 pins (15 & 16) are optional and are only used if the display has a backlight.

The circuit diagram below shows the LCD module with the basic “plumbing” wired up. You will notice that pin 5 (RW) is tied to ground. This pin is use to control whether you are reading or writing to the display. Since reading from the display is very rare, most people just tie this pin to ground.

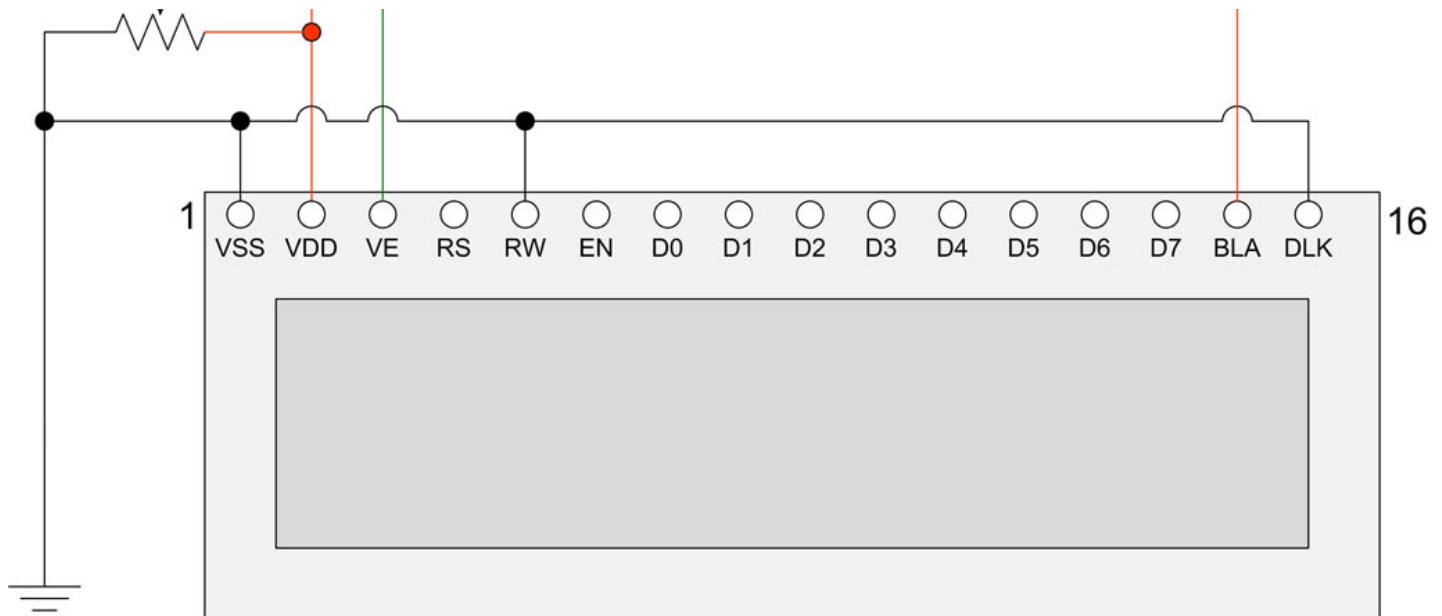The potentiometer connected to pin 3 controls the LCD contrast.



Sending Data and Commands

Data and commands are sent to the module using the 8 data lines (pins 7-14) and the RS line (pin 4). The RS line tells the module whether the 8 data bits relate to data or a command. The data/command is read on the falling edge of the enable line (pin 6). This means that when enable transitions from high to low, the values of D0 to D7 and RS are read.

So to send data or a command to the display, you need to

1. Set Enable to high
2. Set RS and D0-D7 desired values
3. Set Enable to low

There are minimum wait times between these operations, but I won't go into them here. You can look these up in the [LCD Module Datasheet](#). (look at the timing diagrams on page 4)

HD44780 based display modules also have a 4 bit interface mode. Under this mode the data or command is transferred to the module using 2, 4 bit nibbles. This will be discussed in more detail below.

Instructions and Characters

The tables below show the instruction set and character table. Click on a table to get a larger view.





Display	0	0	0	0	0	0	0	0	0	1	Set DDRAM address to 00H.	1.53ms				
Return Home	0	0	0	0	0	0	0	0	1	-	Sets DDRAM address to 00H in AC and returns shifted display to its original position. The contents of DDRAM remain unchanged.	1.53ms				
Entry Mode Set	0	0	0	0	0	0	0	1	I/D	SH	Sets cursor move direction and enable the shift of entire display. These operations are performed during data write and read.	39 μ s				
Display ON/OFF Control	0	0	0	0	0	0	1	D	C	B	Set ON/OFF of entire display (D), cursor ON/OFF(C), and blinking of cursor position character(B).	39 μ s				
Cursor or Display Shift	0	0	0	0	0	1	S/C	R/L	-	-	Moves cursor and shifts display without changing DDRAM contents.	39 μ s				
Function Set	0	0	0	0	1	DL	N	F	-	-	Sets interface data length (DL: 8-bit/4-bit), numbers of display line (N: 2-line/1-line), and display font type (F: 5x11dots/5x8dots)	39 μ s				
Set CGRAM Address	0	0	0	1	AC5	AC4	AC3	AC2	AC1	AC0	Set CGRAM address in address counter.	39 μ s				
Set DDRAM Address	0	0	1	AC6	AC5	AC4	AC3	AC2	AC1	AC0	Set DDRAM address in address Counter.	39 μ s				
Read Busy Flag and Address	0	1	BF	AC6	AC5	AC4	AC3	AC2	AC1	AC0	Reads busy flag (BF) indicating internal operation is being performed and reads address counter contents.	0 μ s				
Write data to CG or DD RAM	1	0	D7	D6	D5	D4	D3	D2	D1	D0	Write data into internal RAM (DDRAM/CGRAM).	43us				
Read data from CG or DD RAM	1	1	D7	D6	D5	D4	D3	D2	D1	D0	Read data from internal RAM (DDRAM/CGRAM).	43us				
Upper 4 bits Lower 4 bits	0000	0001	0010	0011	0100	0101	0110	0111	1000	1001	1010	1011	1100	1101	1110	1111
0000	CG RAM (1)															
0001	CG RAM (2)															
	CG															


[Privacy Preferences](#)
[I Agree](#)

0101	CG RAM (6)													
0110	CG RAM (7)													
0111	CG RAM (8)													
1000	CG RAM (1)													
1001	CG RAM (2)													
1010	CG RAM (3)													
1011	CG RAM (4)													
1100	CG RAM (5)													
1101	CG RAM (6)													
1110	CG RAM (7)													
1111	CG RAM (8)													

Assembling the Circuit


Normally you would drive an LCD display from a microcontroller, computer or similar device. For this exercise we will use just a series of switches. This cuts the interface to the absolute bare essentials.

The circuit being built is shown below.




[Privacy Preferences](#)

I Agree

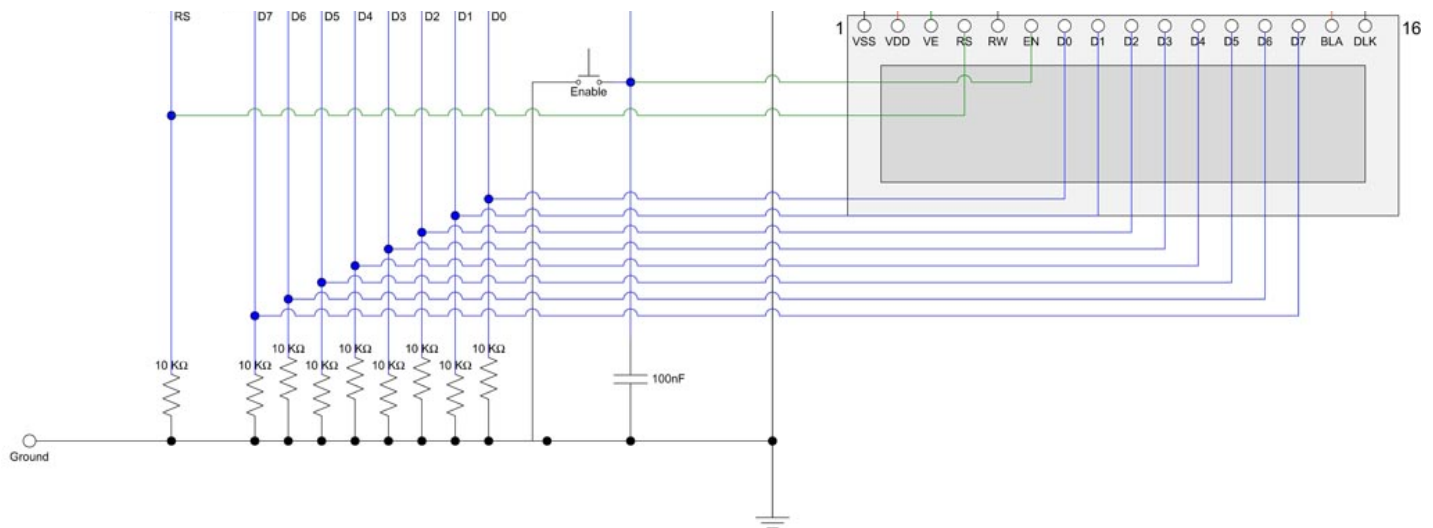


The photo below shows the circuit, on a breadboard without the LCD module. I've also added a small **L7805** based power supply on the right hand side of the board. You can get the parts for the power supply [here](#).

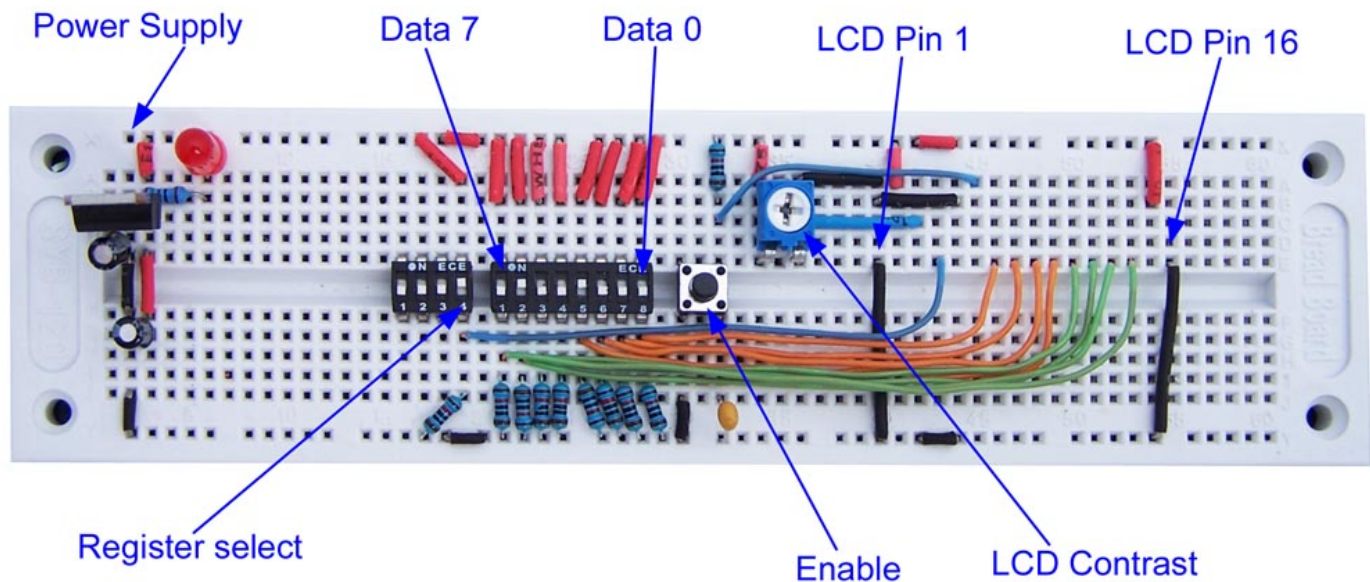The Register Select and data lines are pulled down using a 10K resistor and when the dip switch is closed, those lines go high. The enable line on the other hand is pulled high and when the button is pressed, the line goes to ground. The enable button has a 10nF capacitor to de-bounce it.



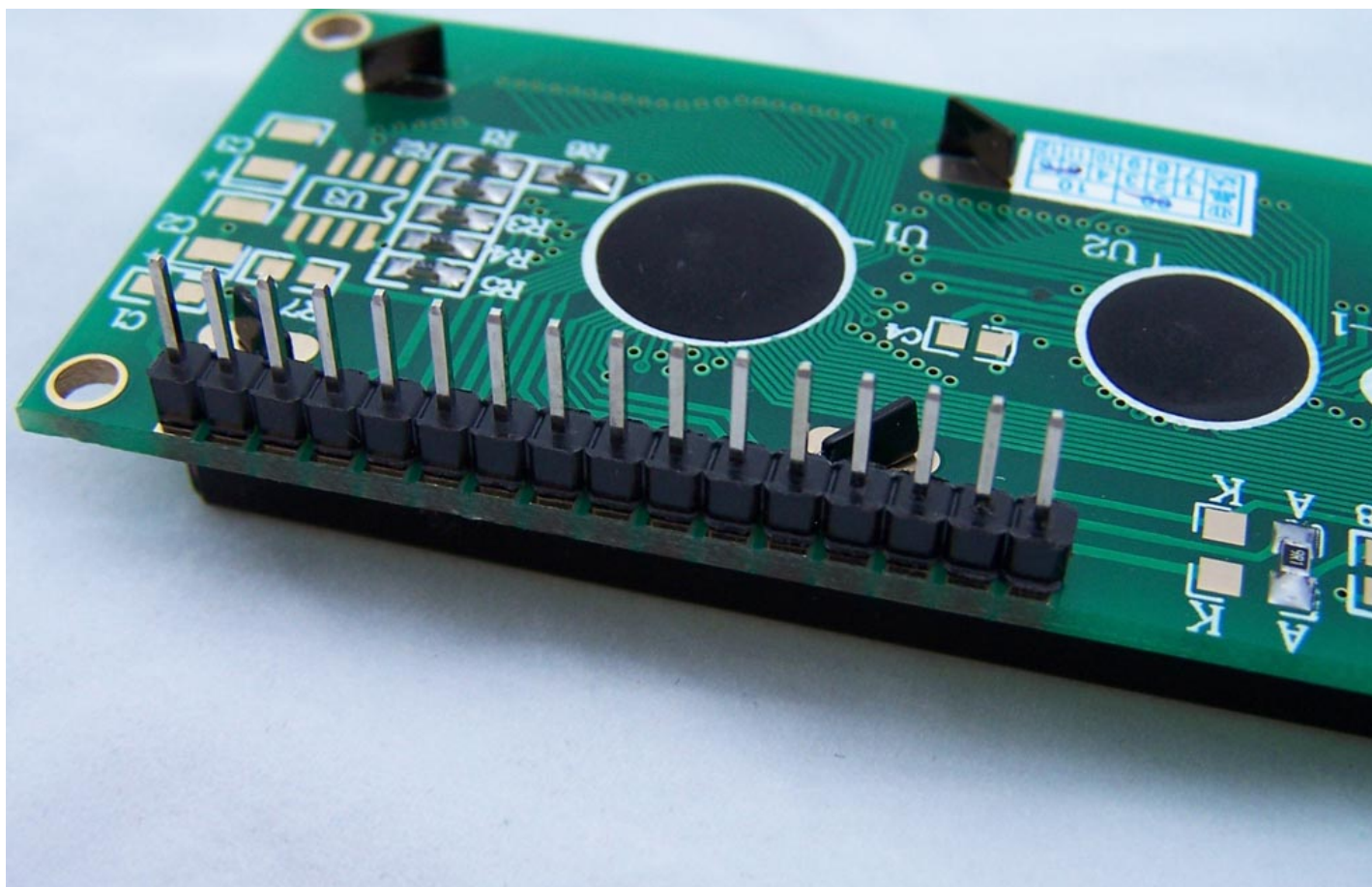
Before inserting the LCD module into the breadboard, you will need to solder a row of 16 pin single row headers. This is shown in the photo below.



Next we insert the LCD module into the breadboard and power it on. When you insert the module into the breadboard, you need to be gentle and work the pins in slowly because the pins are a bit thicker than you would normally use with a breadboard.

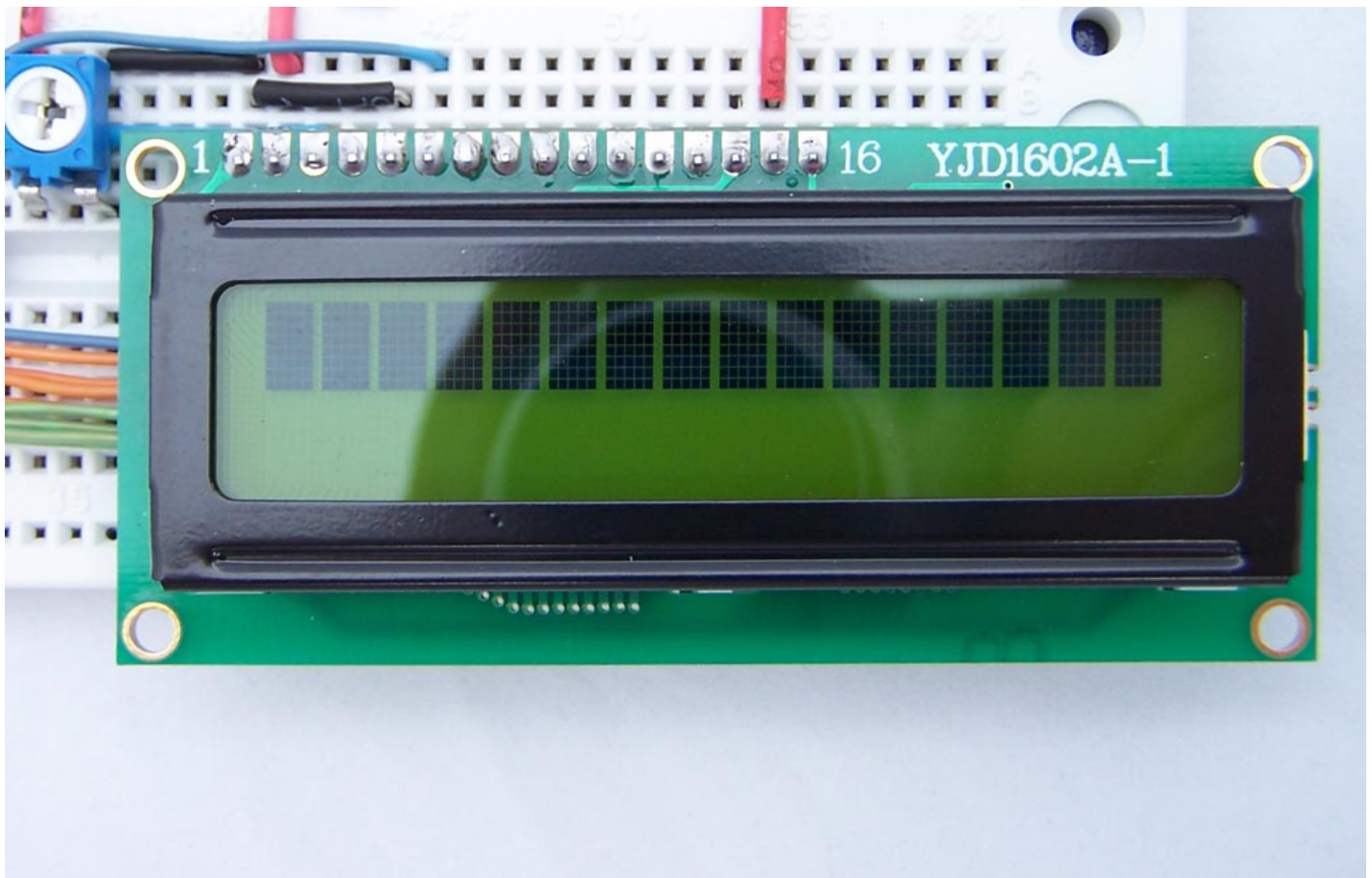If you don't see the pattern shown below, you will need to turn the contrast pot till you do. This pattern is the default pattern for an uninitialized LCD display.





Interfacing via the 8 bit mode

To interface to the display and output text we need to

1. Initialise the display,
2. Set entry mode, and
3. Send a sequence of characters to display

So to output the text “Hello World” we need to power up the device then enter the following sequence of Data/Commands, pressing Enable at the end of each Data/Command block.

RS	D7 to D0	Description
0	0 0 1 1 - 1 0 0 0	Function set, 8 bit, 2 lines, 5×7
0	0 0 0 0 - 1 1 1 1	Display ON, Cursor On, Cursor Blinking





1	0110-1100	/
1	0110-1100	/
1	0110-1111	o
1	0010-0000	space
1	0101-0111	w
1	0110-1111	o
1	0111-0010	r
1	0110-1100	/
1	0110-0100	d

Interfacing via the 4 bit mode

The main benefit of the 4 bit mode is that less data lines are required. In this mode D3 to D0 are tied to ground and data/commands are transferred 1, 4 bit nibble at a time.

RS	D7 to D0	Description
0	0010-0000	Set to 4 bit operation (note: 1 nibble operation)
0	0010-0000	Function set, 8 bit
0	1000-0000	2nd nibble
0	0000-0000	Display ON, Cursor On, Cursor Blinking
0	1111-0000	2nd nibble
0	0000-0000	Entry Mode, Increment cursor position, No display shift
0	0110-0000	2nd nibble



> Privacy Preferences

I Agree



1	0110-0000	<i>e</i>
1	0101-0000	<i>2nd nibble</i>
1	0110-0000	<i>l</i>
1	1100-0000	<i>2nd nibble</i>
1	0110-0000	<i>l</i>
1	1100-0000	<i>2nd nibble</i>
1	0110-0000	<i>o</i>
1	1111-0000	<i>2nd nibble</i>
1	0010-0000	<i>space</i>
1	0000-0000	<i>2nd nibble</i>
1	0101-0000	<i>w</i>
1	0111-0000	<i>2nd nibble</i>
1	0110-0000	<i>o</i>
1	1111-0000	<i>2nd nibble</i>
1	0111-0000	<i>r</i>
1	0010-0000	<i>2nd nibble</i>
1	0110-0000	<i>l</i>
1	1100-0000	<i>2nd nibble</i>
1	0110-0000	<i>d</i>
1	0100-0000	<i>2nd nibble</i>



[Privacy Preferences](#)

I Agree



#ATmega8

#HD44780

#LCD




PREVIOUS ARTICLE

More new products for February

NEXT ARTICLE

Debouncing a switch

RELATED NEWS

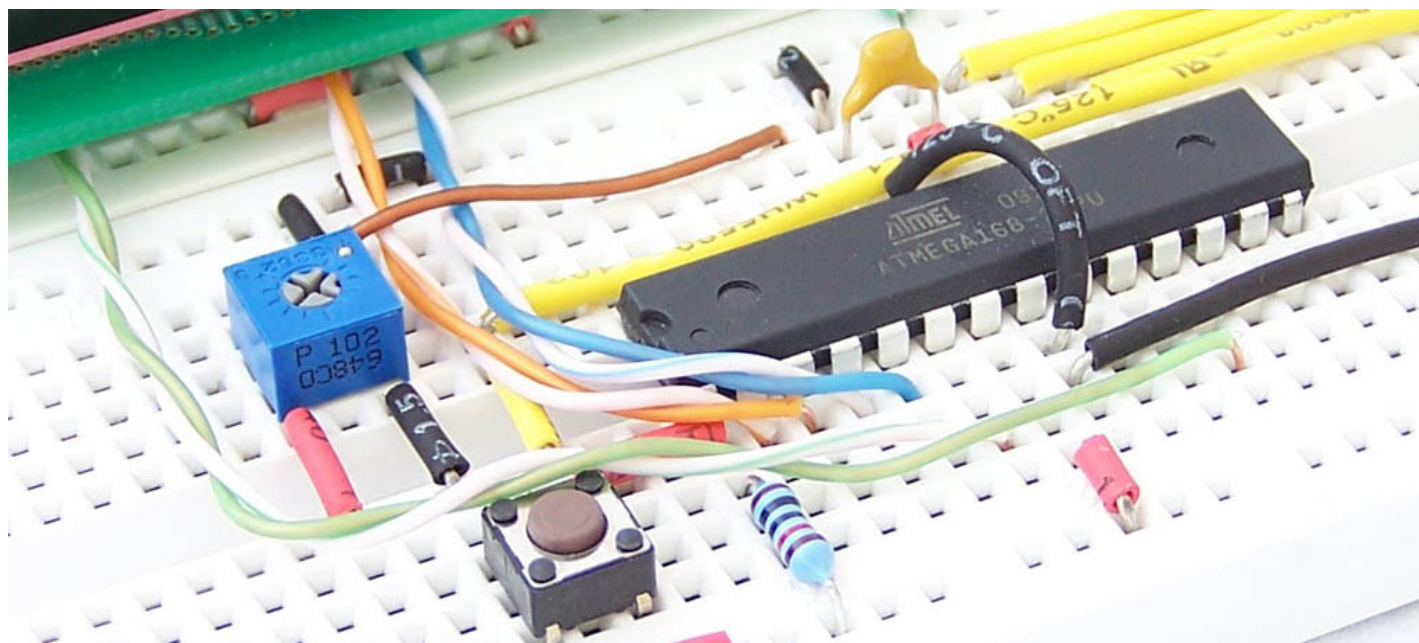


ANALOGUE TO DIGITAL CONVERSION ON AN ATMEGA168

🕒 February 13, 2011



➤ Privacy Preferences

I Agree

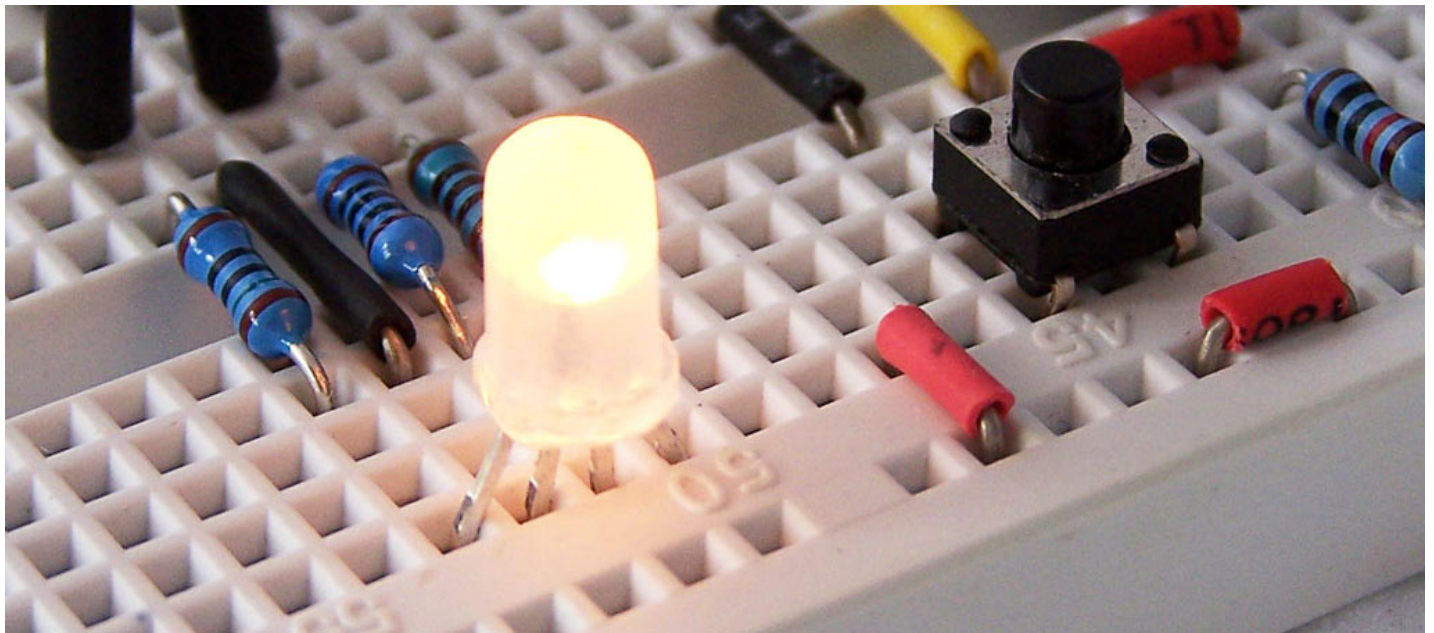


ATMEGA168A PULSE WIDTH MODULATION - PWM

🕒 June 25, 2011

Dimming an incandescent bulb is easy. Simply adjust the current down using a potentiometer and...

READ MORE +

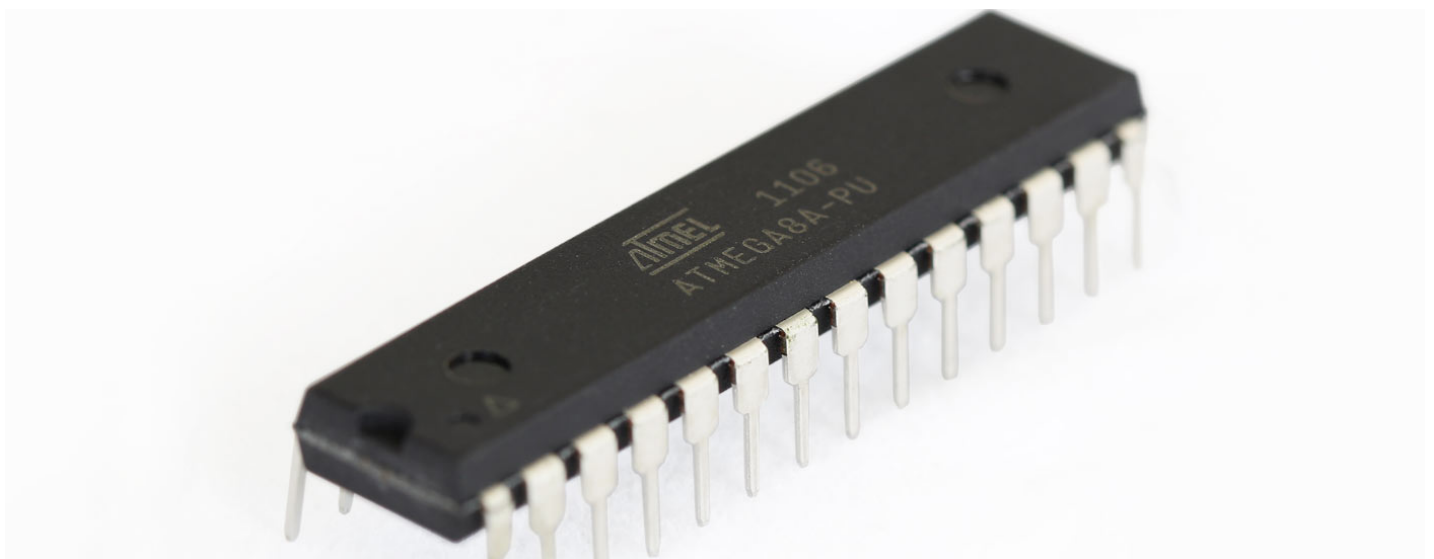

×

➤ Privacy Preferences

I Agree



This tutorial continues on from [Almega8 Breadboard Circuit - Part 1](#) where we build a...

READ MORE +

14 COMMENTS



haren

October 11, 2010 at 11:18 pm

Hi

is lcd initialization same for all lcds available on the market?

because im not using the hitachi one you are talking about im using qp-5515 from jaycar.

thanks heaps

[Reply](#)



raine001@tc.umn.edu

December 8, 2010 at 1:28 pm

there is a data sheet for the qp-5515 here

http://www.jaycar.com.au/products_uploaded/QP-5515.pdf

it looks like a clone of the hd44780 and initialization is the same.

The data sheet does not say much about the contrast voltage; there are a few (mostly older, I think) displays that need a negative contrast voltage. the circuit described above would not produce the rectangular blocks shown on those displays.

[Reply](#)



[Privacy Preferences](#)

I Agree

**kiranvarma-npeducations**

August 23, 2012 at 10:11 am

Really nice about LCD interfacing! its a very neat and clean explanation. thank you for HD quality images feels good while reading the article.

[Reply](#)**Rudolf**

October 17, 2012 at 1:16 am

This is an excellent explanation of this type LCD's functionality and first class combination of text and images. Thank you for these pages.

[Reply](#)**Charlie Mo**

August 19, 2013 at 10:20 pm

Awesome job. Very polished and articulate presentation. Do you have more ? I'd love to see them.

[Reply](#)**Steve**

November 20, 2013 at 8:40 am

Really clear and comprehensive write-up, thanks.

I recently started with Arduino and had a successful play with a 20x4 LCD. Last night I dismantled an old Lexmark printer scanner and, along with a couple of small stepper motors, found an EC016002 LCD. A web surf for info on the LCD brought me here.



**Somnath Das**

August 27, 2014 at 1:26 am

Sir / Madam

My thanks and gratitude for such an excellent explanation of how 16 char LCDs work which even I can understand.

Regards

[Reply](#)**Mihir**

October 11, 2014 at 5:15 am

Thankyou! It works!

[Reply](#)**Ryan O'Connor**

February 11, 2015 at 10:14 am

Really helpful thanks! I love the quality of your photos too. I'll be ordering an lcd and some parts from you soon.

[Reply](#)**lcd recycle**

January 11, 2016 at 1:30 am

Selling

your cracked, damaged and broken LCD screens is essential to staying competitive in the cell phone repair business. Not only do we BUY and SELL broken LCDs, we also offer a LCD swapping service. We Buy Your Cracked, Damaged and Broken LCD Screens...

[Reply](#)[Privacy Preferences](#)[I Agree](#)



[Reply](#)



prs March 19, 2017 at 4:11 pm

learned a lot

[Reply](#)



Kiet June 10, 2017 at 6:13 pm

This is a lot easier to understand than reading the datasheet, thanks for taking time to write this article.

[Reply](#)

LEAVE A REPLY

Your email address will not be published. Required fields are marked *

NAME *

Name *

EMAIL *

Email *

WEBSITE

Website

COMMENT



[Privacy Preferences](#)

[I Agree](#)



SUBMIT

CONTACT US



STAY CONNECTED



INFORMATION



CUSTOMER CARE



PAYMENT OPTIONS



© Protostack Pty Ltd 2016 All Rights Reserved
eCommerce Website developed by Zero Point Labs

> Privacy Preferences

I Agree

